

# Lecture 09: Static Timing Analysis

---

Matthew Guthaus  
Professor

UCSC, Computer Science and Engineering

<http://vlsida.soe.ucsc.edu>

mrg@ucsc.edu



# Today's Topics


---

- Timing Constraints
  - Long paths
  - Short paths
- Static Timing
- Timing Corners


 
# Why Clocks?

- Clocks provide the means to synchronize
  - By allowing events to happen at known timing boundaries, we can sequence these events
- Greatly simplifies building of state machines
- No need to worry about variable delay through combinational logic (CL)
  - All signals delayed until clock edge (clock imposes the worst case delay)



Courtesy K. Yang, UCLA


# Clock Cycle Time

- Cycle time is determined by the delay through the CL
  - Signal must arrive before the latching edge
  - If too late, it waits until the next cycle
    - Synchronization and sequential order becomes incorrect
- Constraint:  $T_{\text{cycle}} > T_{\text{prop\_delay\_through\_CL}} + T_{\text{overhead}}$ 
  - Example: 3.0 GHz Pentium-4  $\square$   $T_{\text{cycle}} = 333\text{ps}$
- Can change circuit architecture to obtain smaller  $T_{\text{cycle}}$

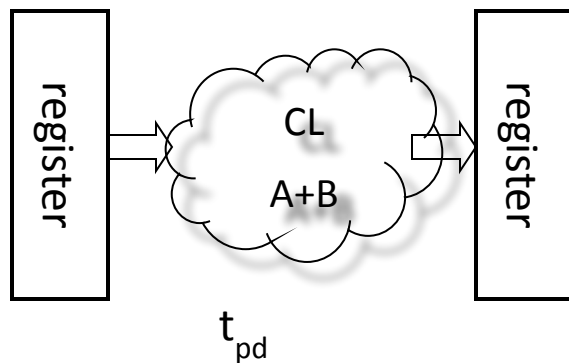
# Pipelining

- For dataflow:
  - Instead of a long critical path, split the critical path into chunks
  - Insert registers to store intermediate results
  - This allows 2 waves of data to coexist within the CL
- Can we extend this ad infinitum?
  - Overhead eventually limits the pipelining
    - E.g., 1.5 to 2 gate delays for latch or FF
  - Granularity limits as well
    - Minimum time quantum: delay of a gate

$$\blacksquare T_{\text{cycle}} > T_{\text{pd}} + T_{\text{overhead}}$$


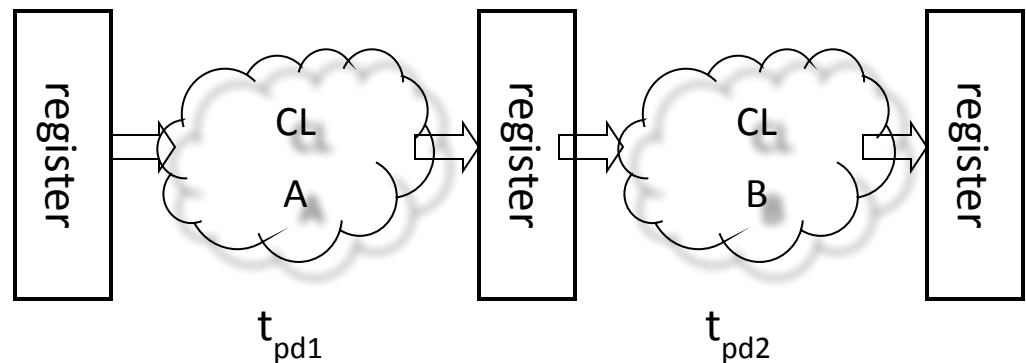
$$\blacksquare T_{\text{cycle}} > \max(t_{\text{pd1}}, t_{\text{pd2}}) + T_{\text{overhead}}$$




Courtesy K. Yang, UCLA



 
# Cycle Time - Setup Time

- For FFs to correctly capture data, must be stable for:
  - Setup time ( $T_{\text{setup}}$ ) before clock arrives



 
$$T_{\text{max}} + T_{\text{setup}} \leq T$$




Courtesy K. Keutzer et al. UCB
 
# Cycle Time – Clock Skew

- If clock network has unbalanced delay – clock skew
- Cycle time is also a function of clock skew ( $T_{skew}$ )



 
$$T_{max} + T_{setup} + T_{skew} \leq T$$





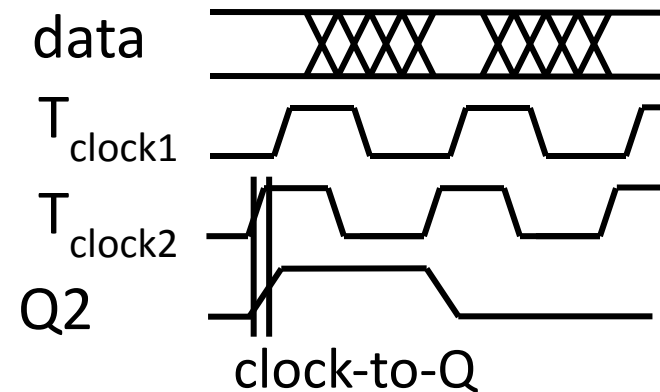
# Cycle Time – Flip-Flop Delay (Clock to Q)

- Cycle time is also a function of propagation delay of FF ( $T_{clk-to-Q}$  or  $T_{c2q}$ )



- $T_{c2q}$  : time from arrival of clock signal till change at FF output

 
$$T_{max} + T_{setup} + T_{skew} + T_{clk-to-Q} \leq T$$




Courtesy K. Keutzer et al. UCB
 
# Min Path Delay - Hold Time

- For FFs to correctly latch data, data must be stable during:
  - Hold time ( $T_{\text{hold}}$ ) *after* clock arrives
- Determined by delay of shortest path in circuit ( $T_{\text{min}}$ ) and clock skew ( $T_{\text{skew}}$ )



 
$$T_{\text{min}} \geq T_{\text{hold}} + T_{\text{skew}}$$



Courtesy K. Keutzer et al. UCB

# Setup, Hold, Cycle Times

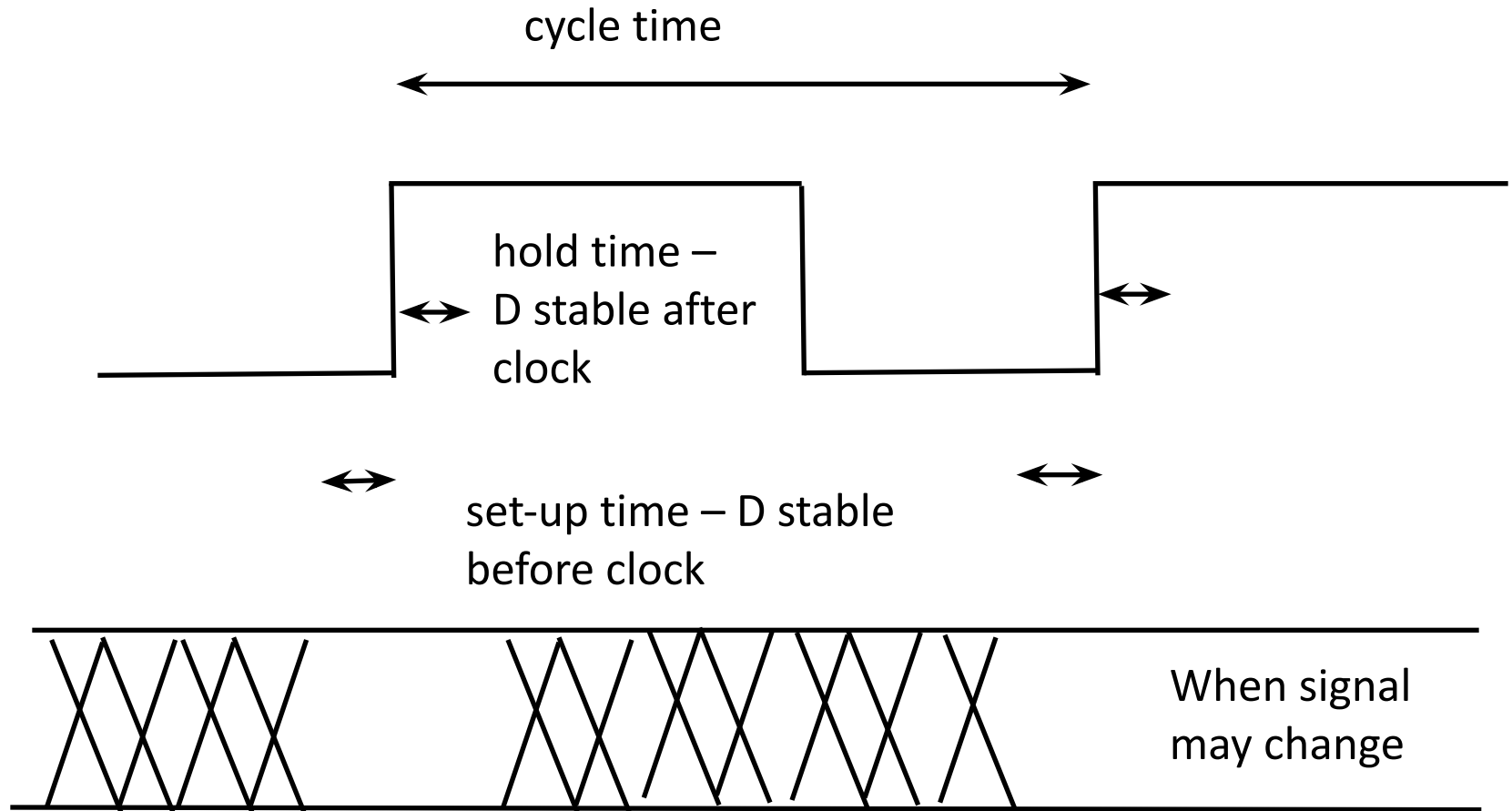

Example of a single phase clock


Courtesy K. Keutzer et al. UCB

# Positive or Negative Clock Skew?

- Usually defined by receiving minus launching clock
- However, often a single value or “budget” can be assumed of  $T_{skew}$ 
  - Used as “worst case” for all pairs of flops
  - Especially if pre-CTS (i.e. during synthesis and placement)
- Technically...
  - Positive skew helps setup paths
  - Negative skew helps hold paths


 
# Timing Constraints for Edge-Triggered FFs




Courtesy K. Yang, UCLA

- $\text{Max}(T_{\text{pd}}) < T_{\text{cycle}} - T_{\text{setup}} - T_{\text{c2q}} - T_{\text{skew}}$ 
  - Delay is too long for data to be captured
- $\text{Min}(T_{\text{pd}}) > T_{\text{hold}} - T_{\text{c2q}} + T_{\text{skew}}$ 
  - Delay is too short and data can race through, skipping a state
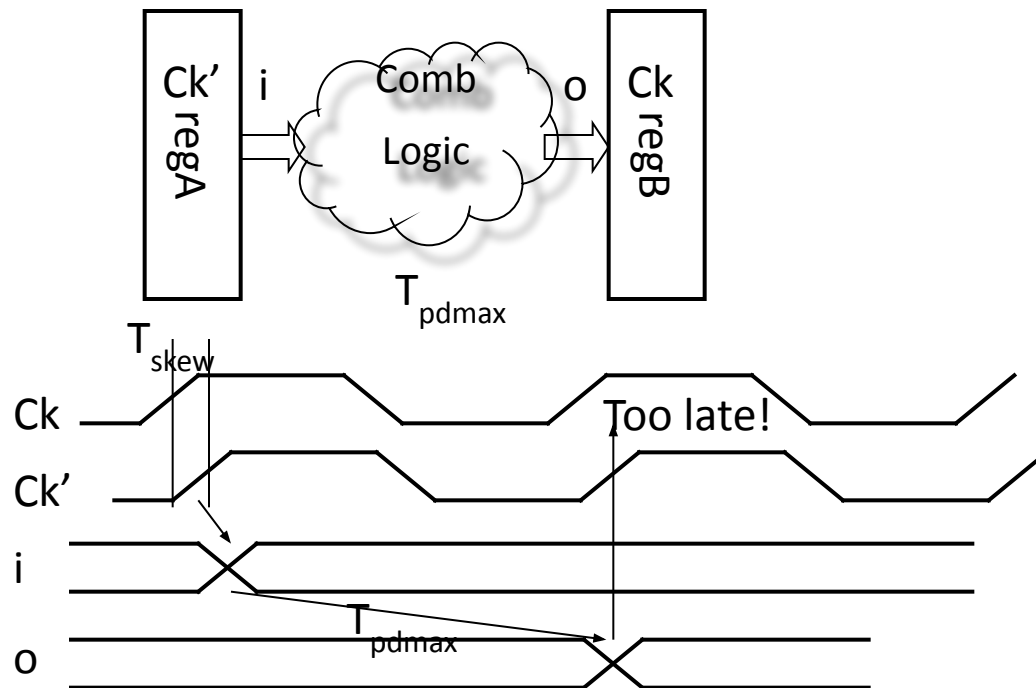
# Example of $T_{pdmax}$ Violation


- Suppose there is skew between the registers in a dataflow (regA after regB)
- “i” gets its input values from regA at transition in  $Ck'$
- CL output “o” arrives after  $Ck$  transition due to skew
- To correct this problem, can *increase* cycle time



Courtesy K. Yang, UCLA
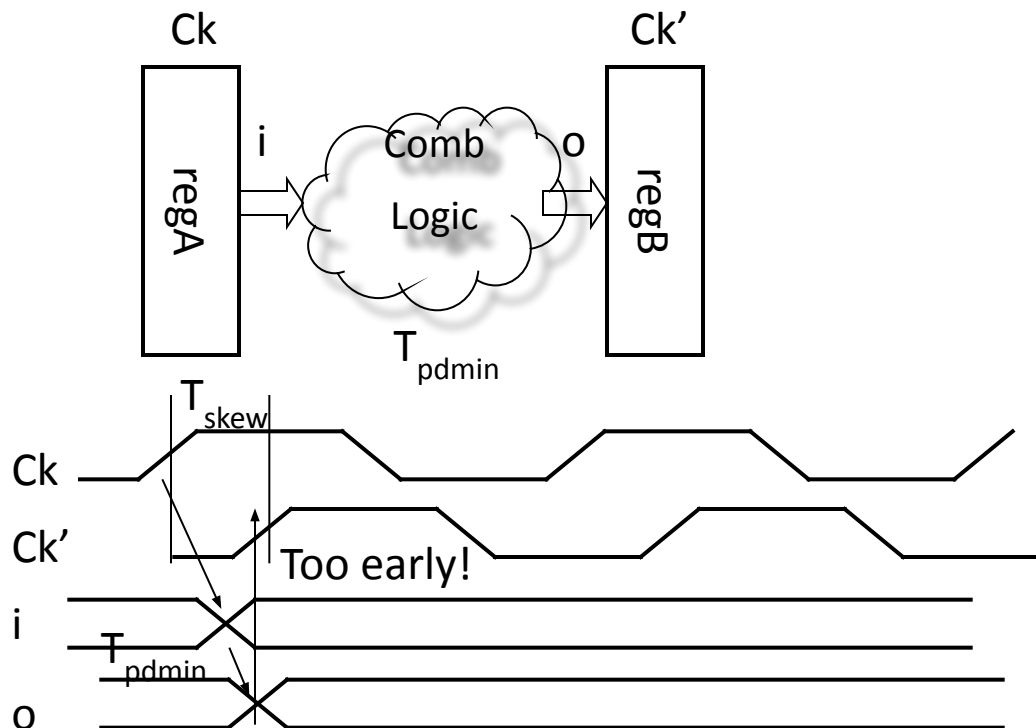
# Example of $T_{pdmin}$ Violation: Race Through

- Suppose clock skew causes regA to be clocked before regB
- “i” passes through the CL with little delay ( $t_{pdmin}$ )
- “o” arrives before the rising Ck’ causes the data to be latched
- Cannot be fixed by changing frequency □ have rock instead of chip



Courtesy K. Yang, UCLA

# Summary: Timing Constraints

- Synchronous design  
= combinational logic  
+ sequential elements


- For each flip-flop:

- $T_{max} + T_{skew} + T_{setup} < T_{cycle}$

- $T_{min} > T_{hold} + T_{skew}$

- $T_{max}$ : longest data propagation path delay

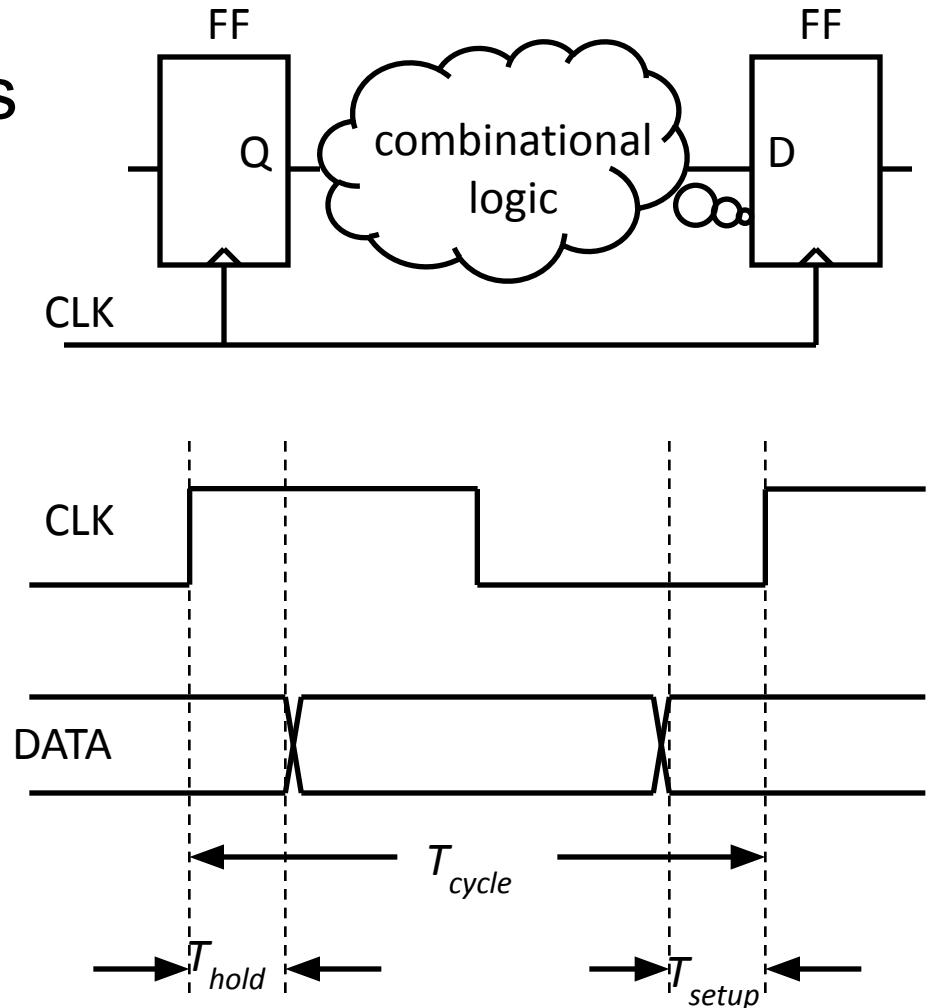
- $T_{min}$ : shortest data propagation path delay




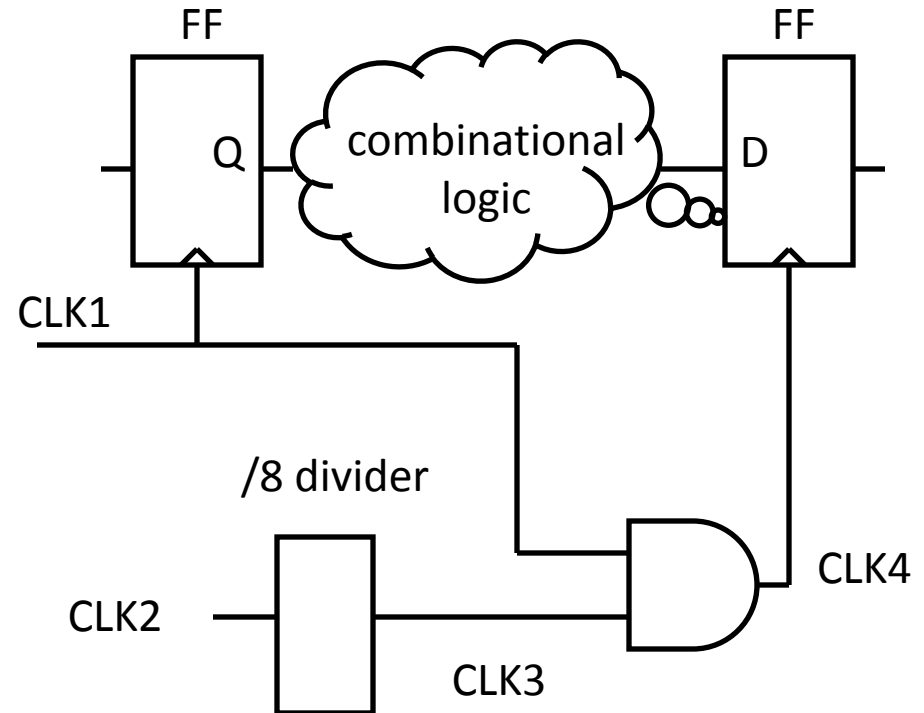
# Clock Identification

- Partition the design
- Clock network
  - Clock definition
  - Derived clock
  - Clock groups
  - Clock delay (skew) calculation
  - Timing constraints exist between clocks with a common divisor frequency
- Data paths with timing constraints





# STA Overview

- Questions it can answer
  - Can my circuit run at X Ghz?
  - What is the worst path of my circuit?
  - Do I have any hold violations?
- Static vs Dynamic Timing
  - For n inputs and m FF bits, there are  $2^{(m+n)-1}$  possible patterns.
  - This cannot be exhaustively tested!
- Incremental timing for optimization
  - If I have a timing problem, how do I fix it?
- Corner analysis for temperature, process, etc.
  - Will my circuit work under all conditions?


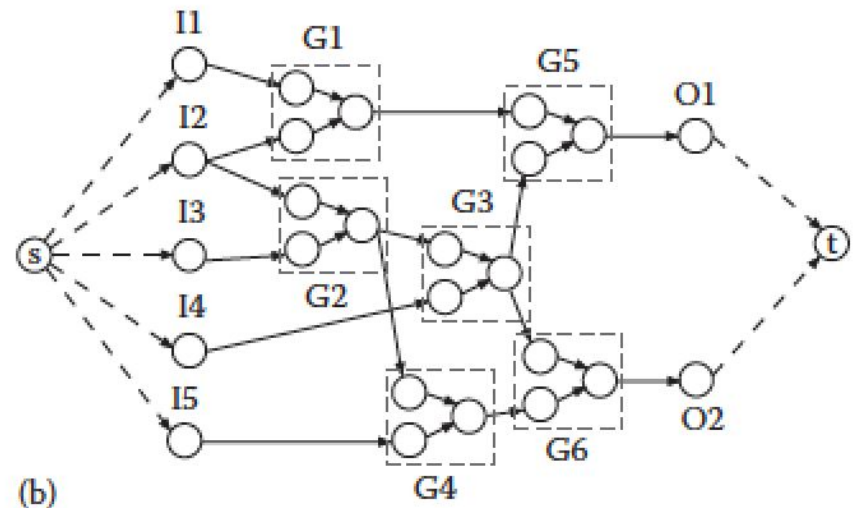 
# Circuit Representation

- Directed Acyclic Graph (DAG)
  - Circuit is broken at sequential elements (e.g. FFs)
  - s can be circuit input or FF output (input delay)
  - t can be circuit output or FF input (setup time)
- Edges are gate or wire delays
- Nodes are pins on gates or inputs/outputs



# Gate Delay Models


---

- Discussed in Cell Library lecture
- Use as inputs:
  - output load
  - input signal slew (transition time)


 
# Capacitance

- Lumped capacitance
  - Self loading capacitance
  - Fanout gate pin capacitances
  - Fanout wire substrate/coupling capacitances
  - More on crosstalk later
- Effective capacitance
  - Not all capacitance is seen at the output due to “resistive shielding”
  - Usually a Pi (or T) model



# Wire Delay Models

---

- Wire delay from driver pin to each fanout gate pin
- **More in Interconnect lecture...**



# Block Based Timing Analysis


---

- Ignores function of gates
- Propagates the worst cumulative delay from inputs to outputs
- Based on 1966 project management technique: Program Evaluation and Review Technique (PERT)


 
# Arrival Time

- Typically compute for (Rise, Fall) x (Early, Late)
- Also propagate slew (delay needs the slew)



```
# Assume all inputs come from a DFF
set_driving_cell -lib_cell $DFF_CELL [all_inputs]
set_input_delay $DFF_CLKQ -clock $CLK [remove_from_collection [all_inputs] [list $CLK $RST]]
```






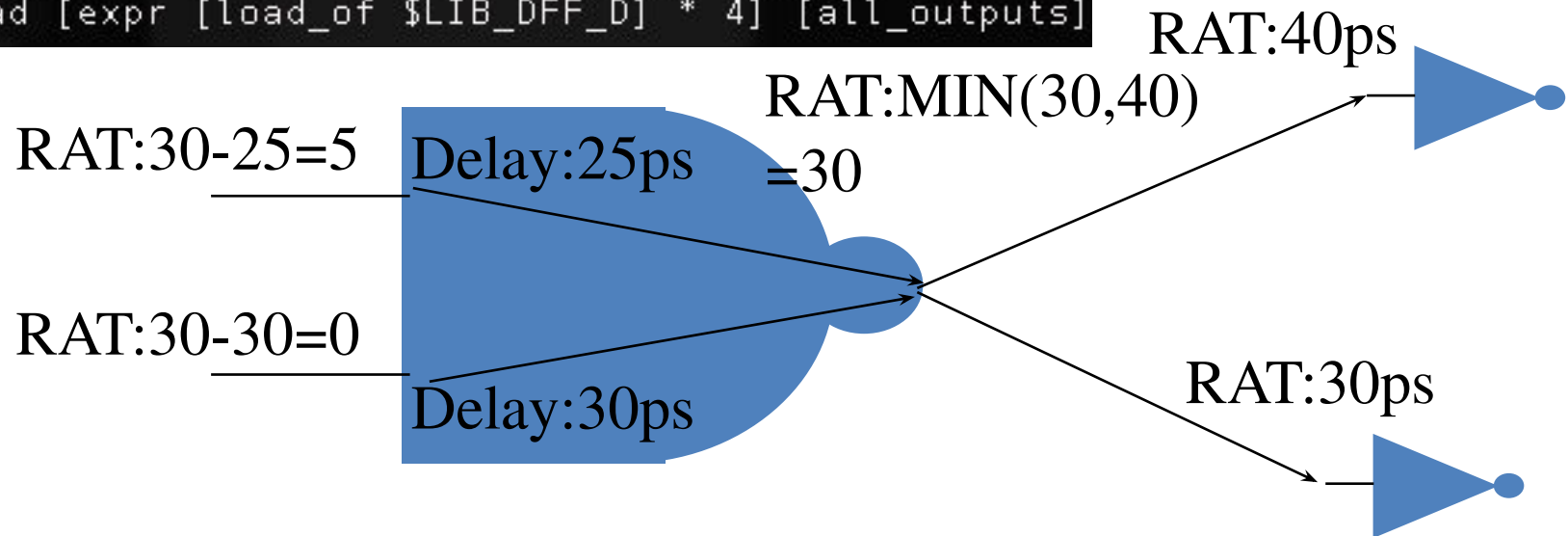
# Required Arrival Time

- Time signal is needed at a point to get to output by constrained time
  - Late checks set RAT to clock period at outputs/FFs
  - Early checks set RAT to hold time at output/FFs
- Typically compute for (Rise, Fall) x (Early, Late)

```
# Create an F04 output load with 4 DFFs
set_output_delay $DFF_SETUP -clock $CLK [all_outputs]
set_load [expr [load_of $LIB_DFF_D] * 4] [all_outputs]
```




# Required Arrival Time

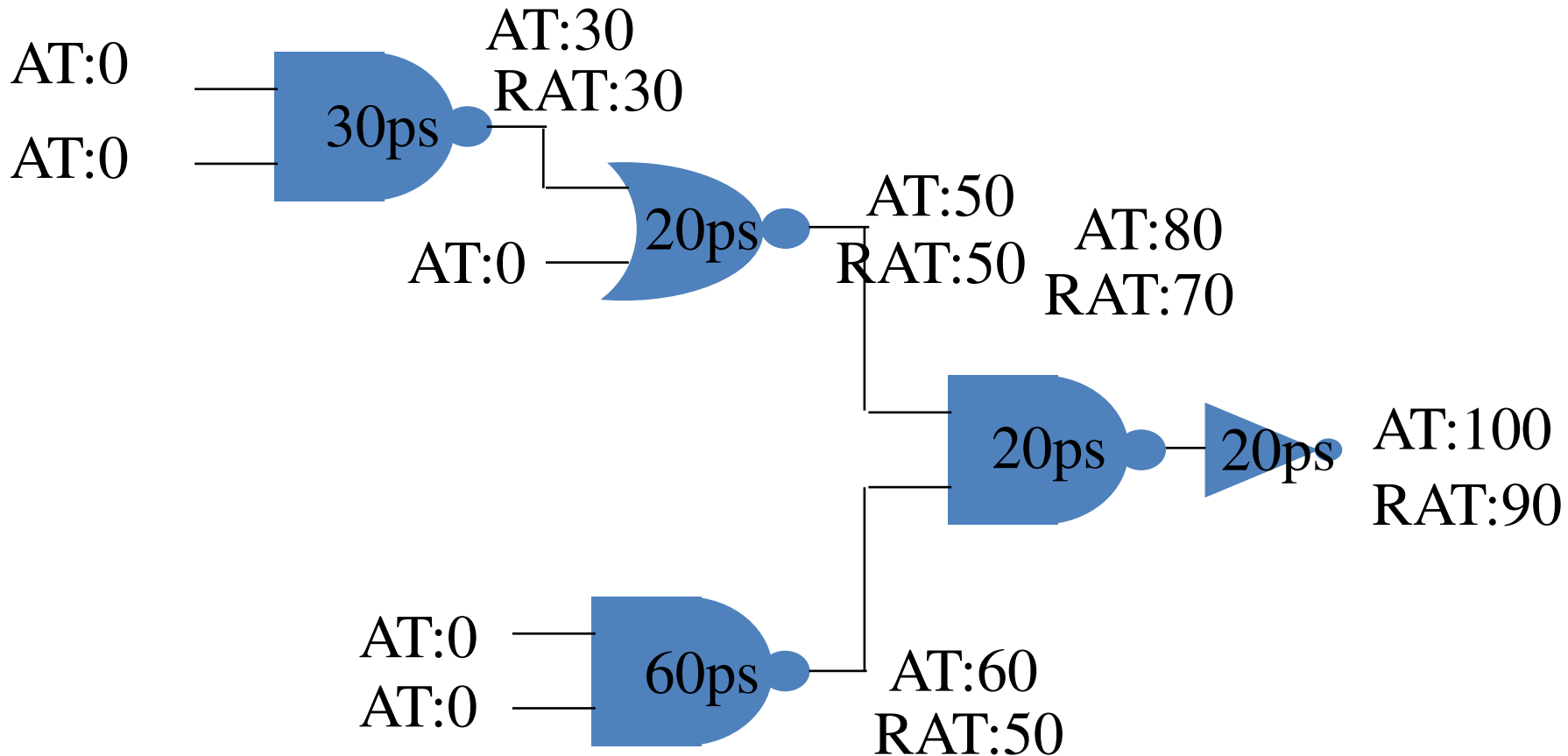

← RAT: Min of all outputs...



# Slack: RAT-AT

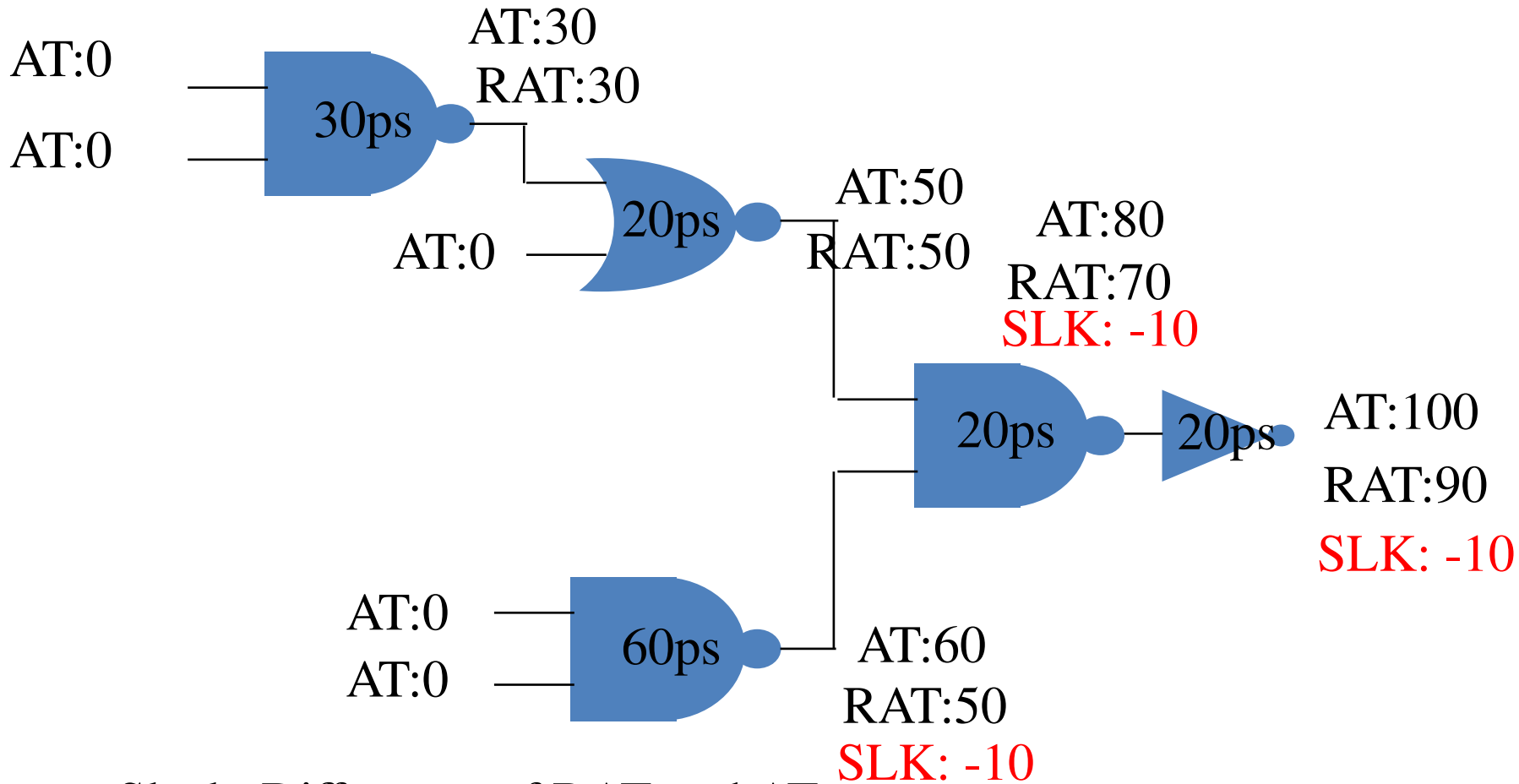

Slack: Difference of RAT and AT


# Transition Time/Slew Propagation

- The above talked about wire and gate delays, but we also must propagate slew to every wire.
- What slew do we propagate?
  - Biggest slew of all inputs? Could be conservative if it is too early.
  - Latest arriving signal? This may not determine the worst delay.
  - Selectable in STA:
    - set timing\_slew\_propagation\_mode worst\_value



 
# Slew Challenge Example

- Remember: Delay is 50%-50%, Slew is 10%-90%
- Signal A may have a bigger delay, but B has such a bad slew that it determines the output delay



A determines delay

 

B determines delay  
despite arriving earlier  
than A




# Other Delay Assumptions

- Single input switching assumption
  - Could turn on multiple paths in CMOS network which result in ramp with two different slopes
  - Switching a second input could add internal gate capacitance to output
- Slew is a single ramp
  - If second path in network turns on...
  - Inductance can have non-monotonic behavior


 
# Timing Corners

- The previous gate and wire delays can also have different “corners”
  - Temperature
  - Process (PMOS/NMOS variation)
  - Supply Voltage
- Worst case corners
  - Early will want to use the fastest process, highest supply, lowest temperature
  - Late will want to use the slowest process, lowest supply, highest temp
- Worst case corners are becoming too pessimistic!





# Demo in OpenRoad/OpenLane

---

Text STA reports

Hold

Setup

Corners

GUI browser

